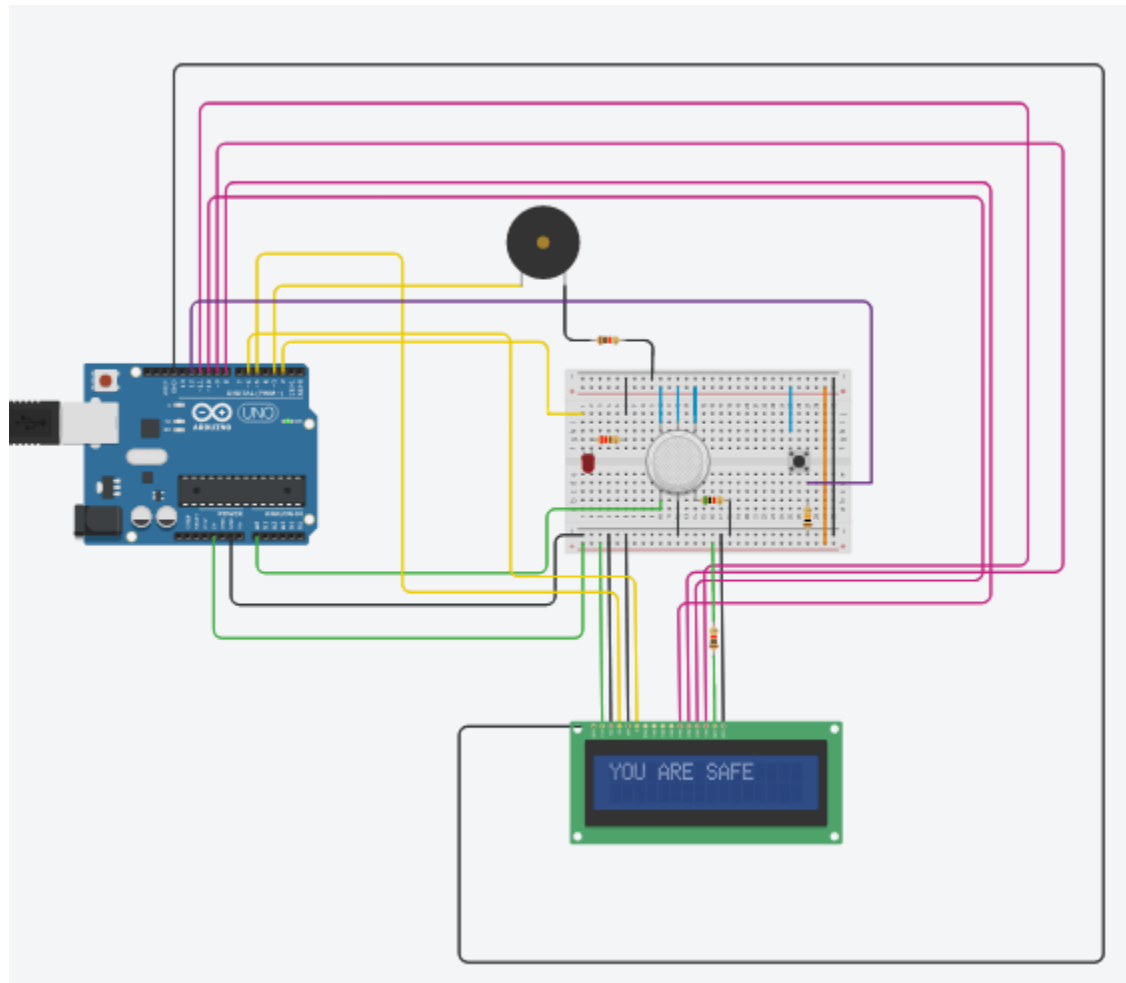




# Internet of Things

Smoke Detection System in TinkerCAD

## Design in TinkerCad



## Arduino Sketch

```
#include <LiquidCrystal.h>
LiquidCrystal lcd(5,6,8,9,10,11);


int state =0;
int sensorThresh = 400;

void setup()
{
  pinMode(2, OUTPUT);
  pinMode(3,OUTPUT);
  pinMode(4,INPUT);
  pinMode(A0,INPUT);
  Serial.begin(9600);
  lcd.begin(16,2);
}

void loop()
{
  int analogValue = analogRead(A0);
  Serial.print(analogValue);
  state = digitalRead(2);
  if(analogValue>sensorThresh)
  {
    digitalWrite(2,HIGH);
    tone(3,1000,10000);
    lcd.clear();
    lcd.setCursor(0,1);
    lcd.print("DANGER ALERT");
    delay(500);
    lcd.clear();
    lcd.setCursor(0,1);
    lcd.print("EXIT NOW");
    delay(500);
  }
  if(analogValue<sensorThresh || state == HIGH)
  {
    digitalWrite(2,LOW);
    noTone(3);
    lcd.clear();
    lcd.setCursor(0,0);
    lcd.print("YOU ARE SAFE");
    delay(1500);
    lcd.clear();
  }
}
```

```
    lcd.setCursor(0,1);  
    lcd.print("NO WORRIES");  
    delay(1500);  
  }  
}
```

## Circuit schematic

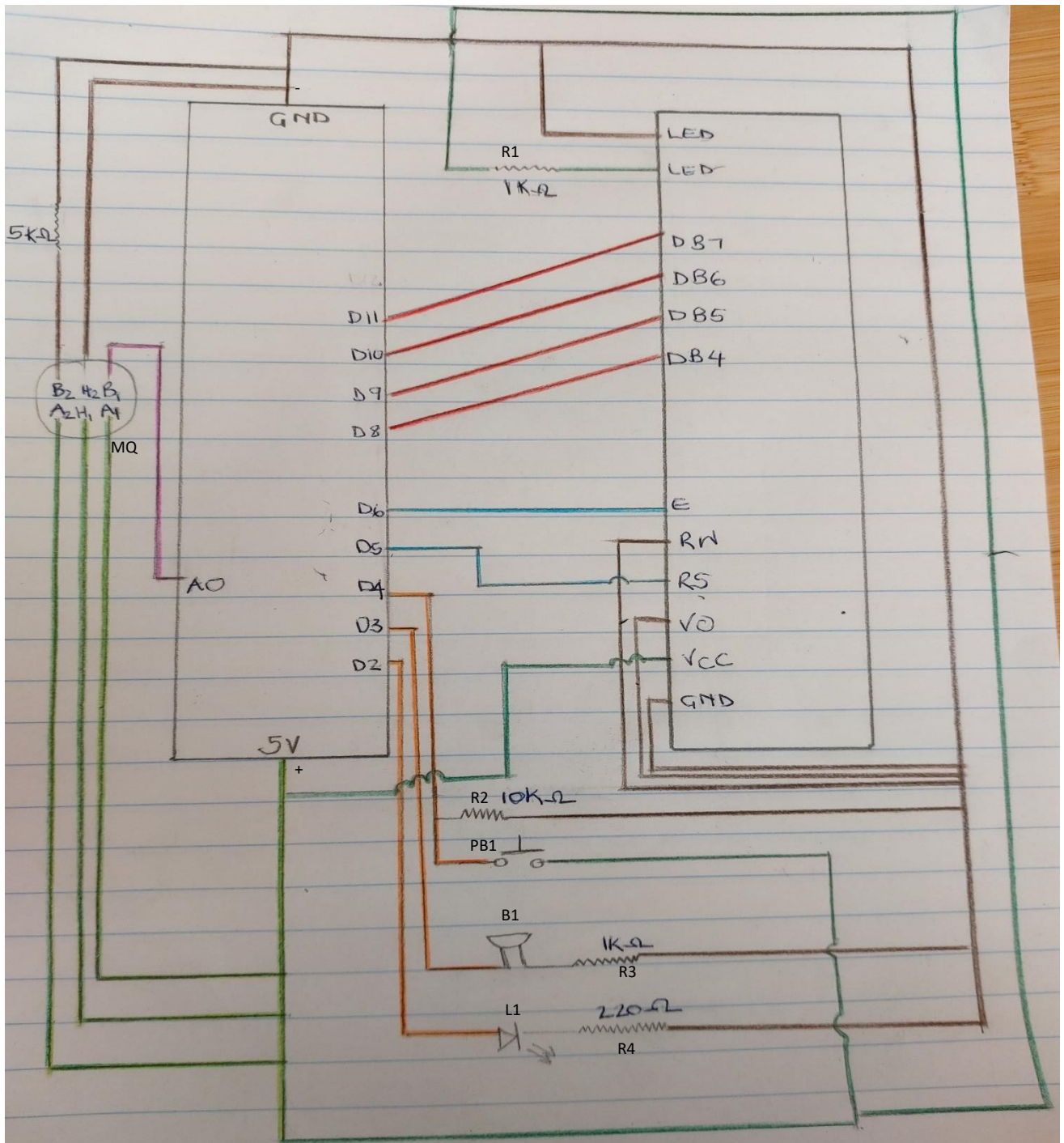

## System Description

Resistors: 220ohm Resistor, 10kilo ohm Resistor, 5kilo ohm Resistor, 2 x 1kilo ohm Resistor

Component	Role
<b>Arduino Uno R3</b>	An open source microcontroller that uses an ATmega328 microchip, a 16 MHz resonator, a USB connection, a power jack, an in-circuit system programming (ICSP) header, and a reset button.
<b>16x2 LCD</b>	Displays warning messages
<b>MQ2 Gas Sensor</b>	Connects to the analog pin and detects H2, LPG, CH4, CO, Alcohol, Smoke or Propane. Highly sensitive and leads to fast response time. Connected to the Arduino Uno through the Analog pin.
<b>Normally Open Pushbutton</b>	Open(low) until it is pressed, connected to the Arduino Uno R3 through a digital pin, pulled down by a 10Kilo ohm resistor
<b>Red LED</b>	Grounded a 220ohm resistor, connected to the Arduino by a digital pin